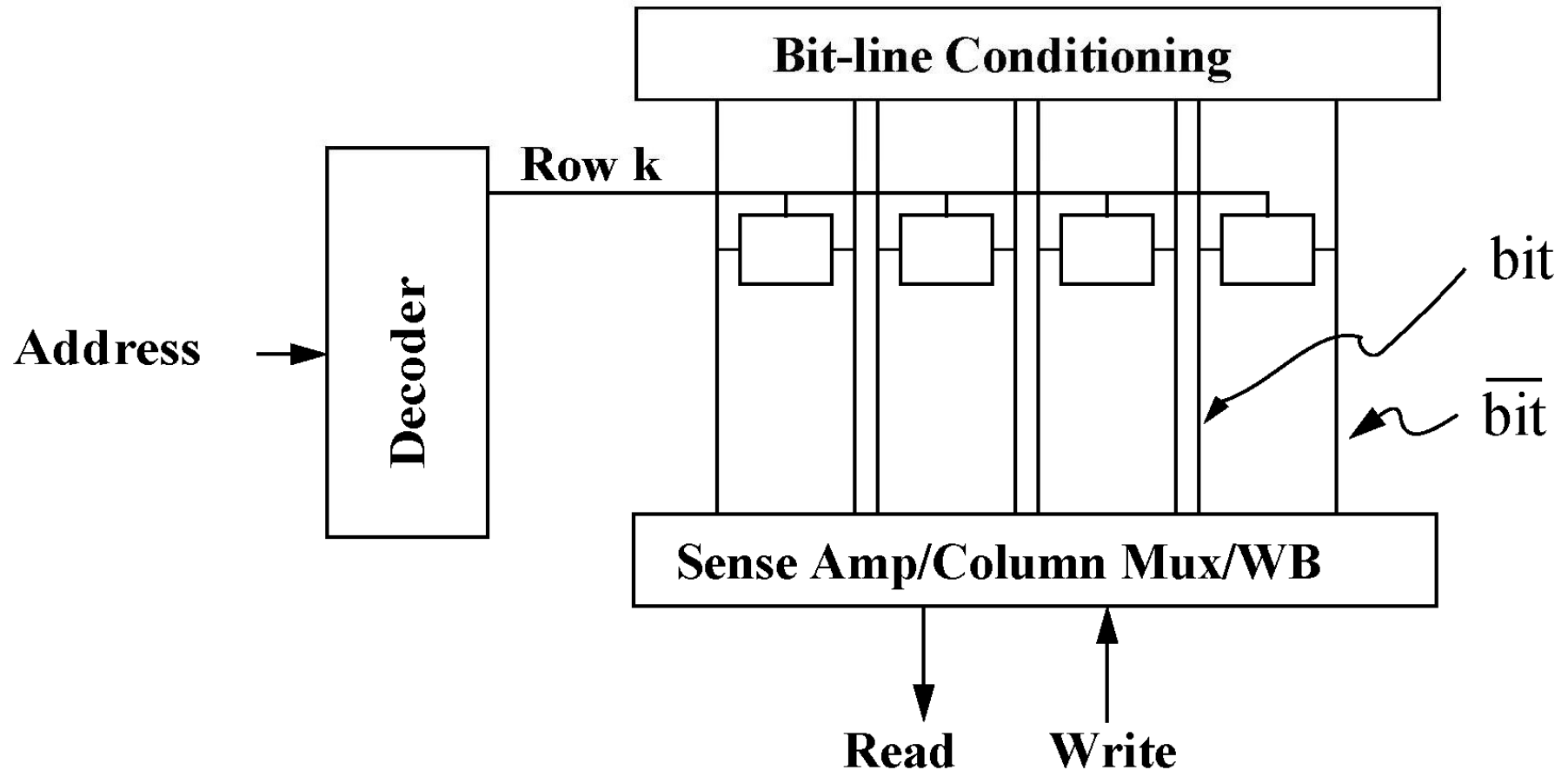


ECE 6130
VLSI and Advanced Digital Design

Memory


RAM Organization



- **Data is carried on complementary bit busses**
- **Cell design must consider analog behavior**

SRAM Cell

 - SRAM cell is designed for density, power, and speed
- Basic cell uses 6T




- SRAM transistor β s are critical

SRAM Operation

- The key issue in an 6T SRAM is how to distinguish between read and writes.
- There is only one wordline, so it must be high for both reads and writes. The key is to use the fact there are two bitlines.
- Read: Both Bit and Bit_b must start high. A high value on the bitline does not change the value in the cell, so the cell will pull one of the lines low
- Write:
 - One (Bit or Bit_b) is forced low, the other is high
 - This low value overpowers the pMOS in the inverter, and this will write the cell.



Transistor Sizing

 - For the cell to work correctly a zero on the bit line must overpower the pMOS pullup, but a one on the bit line must not overpower the pull down (otherwise reads would not work)




- For the pull down M3 is passing a zero, so for it to overpower the pMOS it must be at least as wide (preferably 1.5x as wide). This gives a 2-3:1 current ratio between the nMOS and the pMOS.
- For pull up M3 is passing a one so it is somewhat weaker. Still M3 should be 1.5 to 2x smaller than M1 to make sure a read does not disturb the value of the cell.

Common Layout

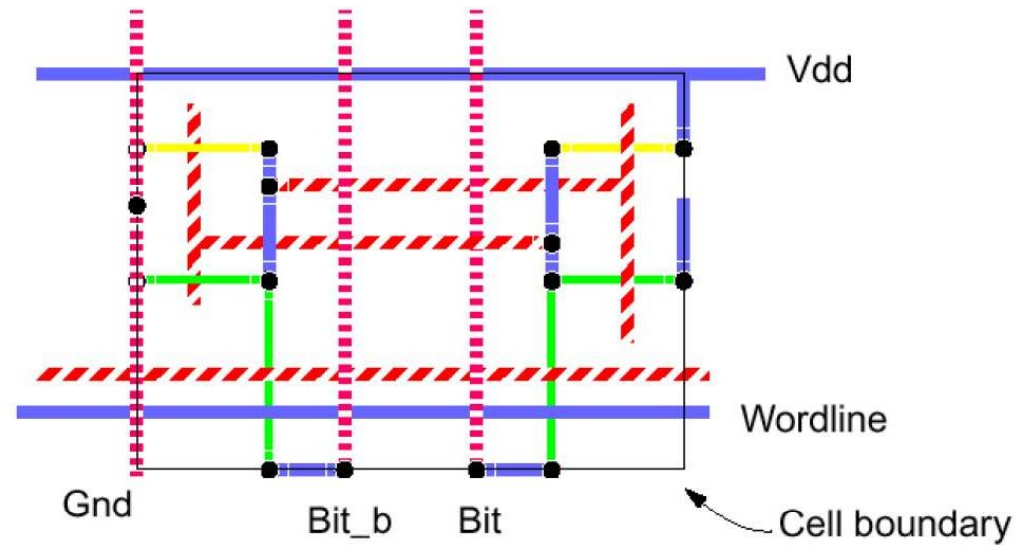 



SRAM Read

 - Read operation is performed by sense amplifier. As Bit and $\overline{\text{Bit}}$ diverge, the sense amp will detect the divergence and amplify the difference.
- Sense amp is usually implemented with a differential amplifier.



DRAM

- Basic DRAM is 1T1C design:

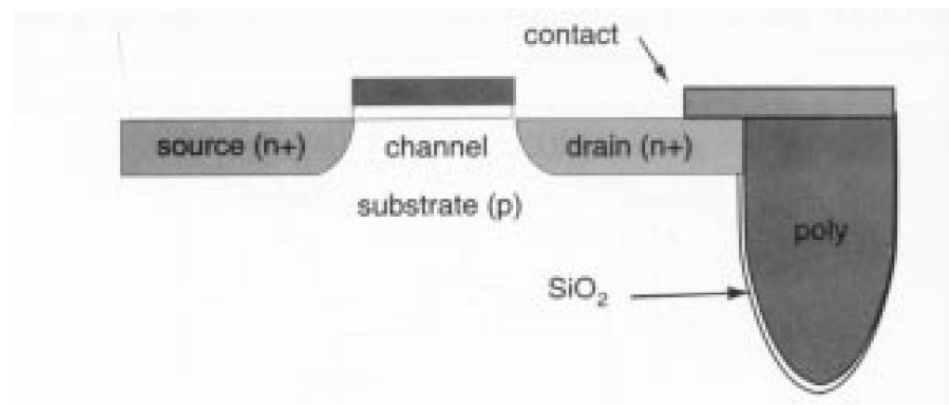 


- Capacitor is special vertical trench design

DRAM Quirks


- **Leakage current means stored value will decay over time (stable for several ms)**
 - necessity for refresh
- **Read is destructive**
 - Data must be written back to a row of DRAM after it is read
- **Because of the very fine horizontal pitch of a DRAM cell (few λ), a DRAM row is many times wider than the output row of the array.**
 - The column address selects which column of the array will be accessed
- **Historical pin limitations**
 - row and column addresses multiplexed on address bus and latched by $\overline{\text{RAS}}$ and $\overline{\text{CAS}}$ signals

Typical DRAM Timing

- Read timing

 

- Write timing

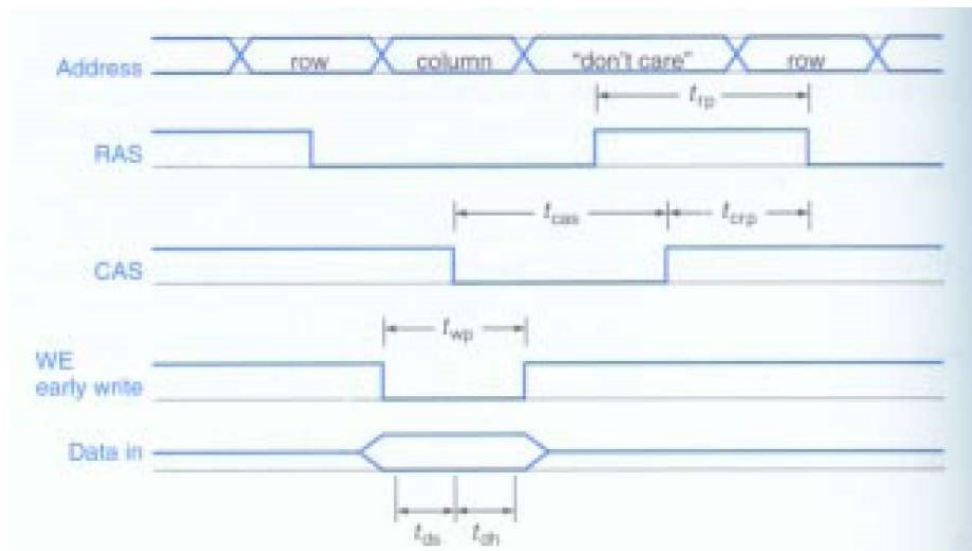


Details

- **Write is really**
 - read row into row buffer
 - modify word selected by column address
 - write modified row back
- **Refresh cycle is read-nomodify-writeback**
- **Throughput and access latency is limited by combinational delays through row decoders, access of row, and column select**
- **Burst mode: for a given row address, sequence through successive column addresses accessing data already in row buffer**


Modern DRAM

- **SDRAM**
 - synchronous, pipelined design
 - several banks
 - output delayed by multiple cycles
 - addressing similar to older DRAM
- **RDRAM**
 - Rambus DRAM
 - synchronous
 - many banks
 - packet switched internal network
 - low voltage signalling interface

Example SDRAM Timing

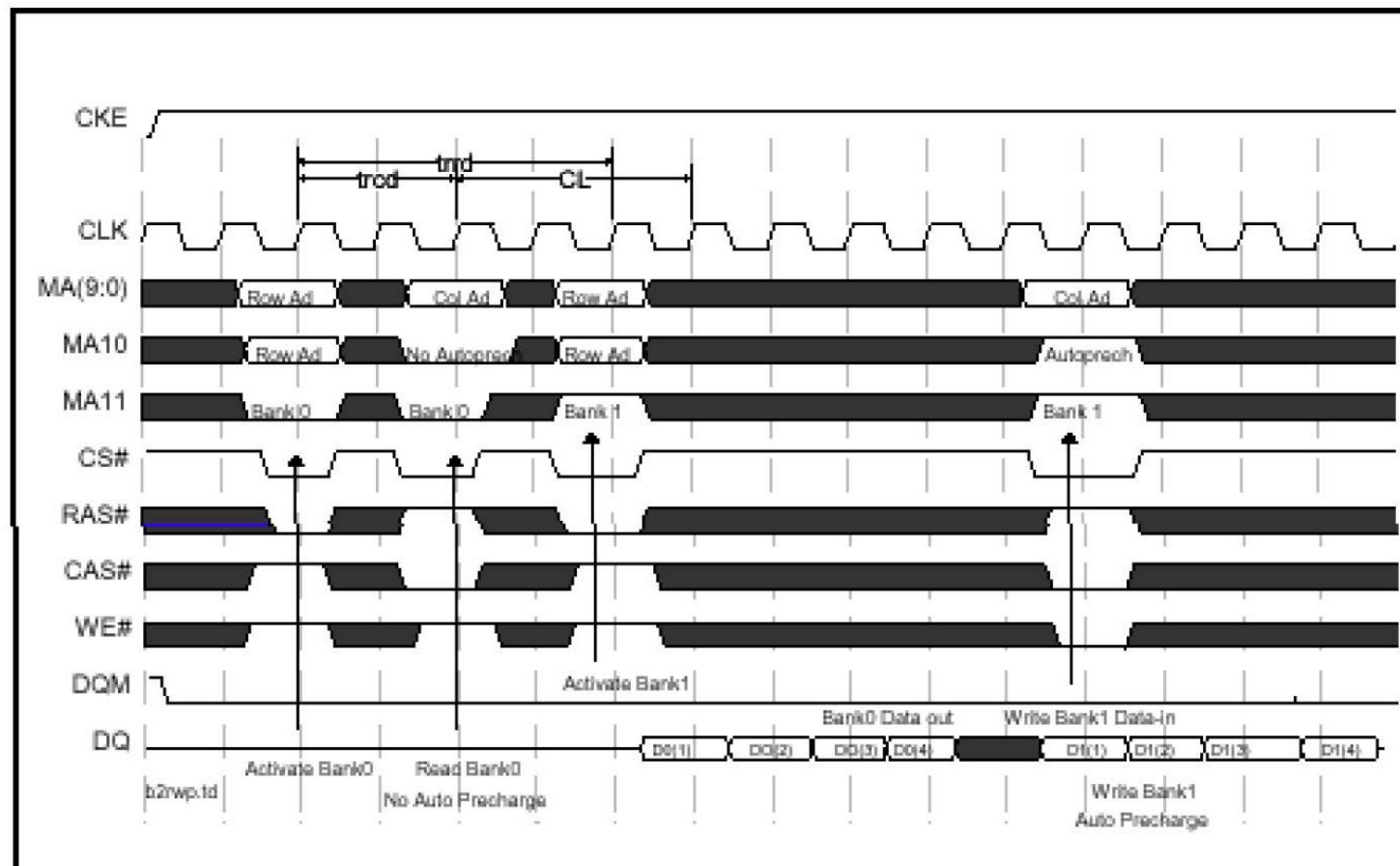

RDRAM Architecture

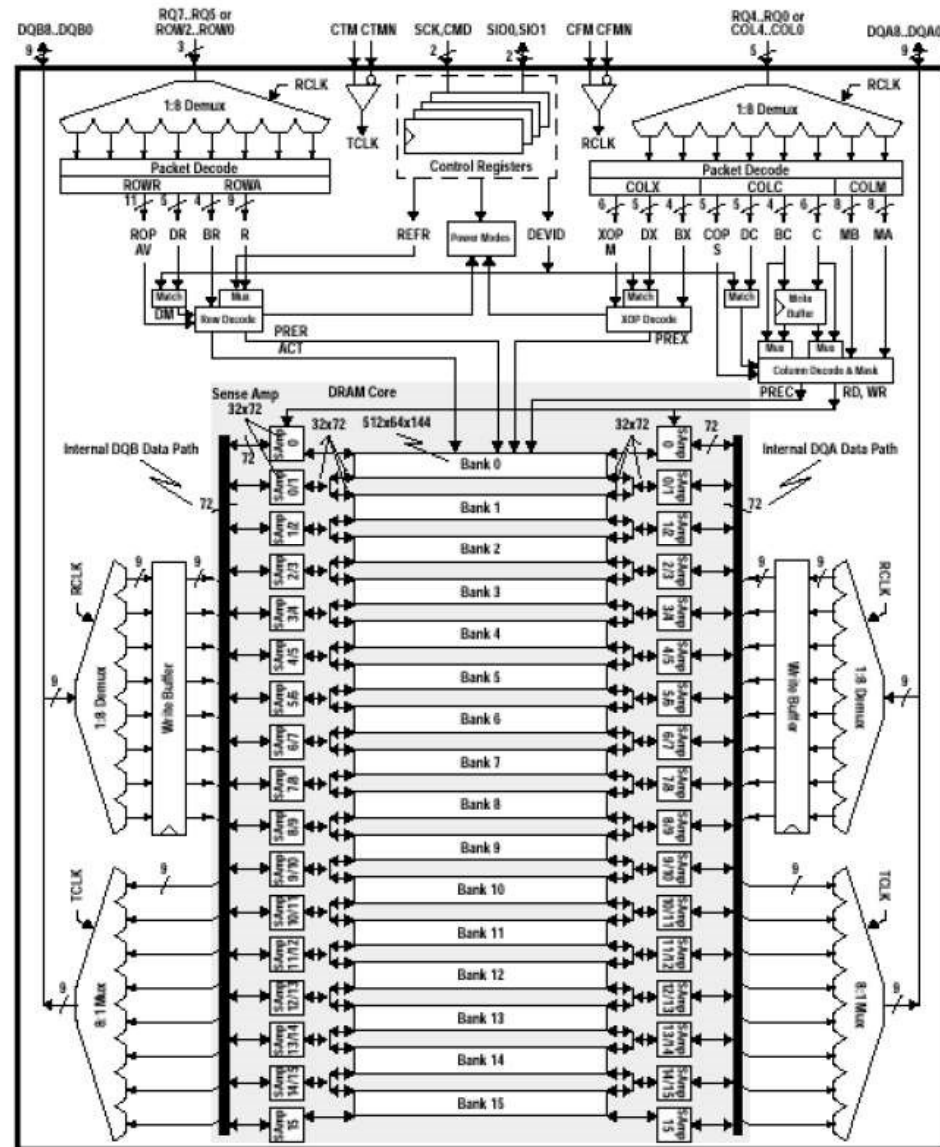

Example RDRAM Access

