

ECE 3060


VLSI and Advanced Digital Design

Hazards

Motivation


Suppose we wish a logic signal (say a DRAM $\overline{\text{WE}}$ signal) to be glitch free

 Suppose the signal is generated by four states of a state machine as shown



Minimization yields $\overline{\text{WE}} = (s_2 s_0 + s_2 s_1)$


Implementation

 


Consider transition $S = 111$ to $S = 011$

This cause of this glitch is a static 1 hazard in the implementation.

 
A static 1 hazard is present whenever adjacent 1 nodes on the cube are not covered by the same implicant



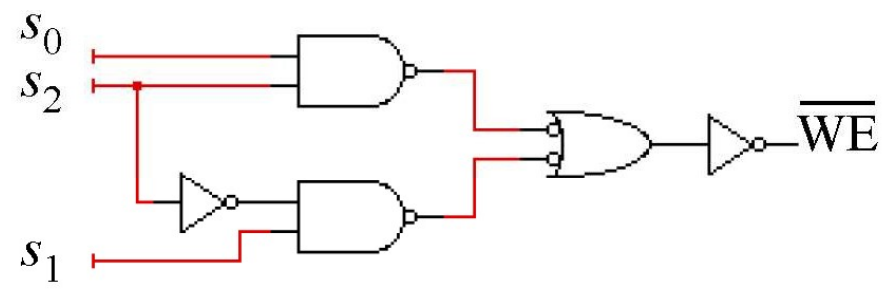

Solution

Add the consensus term $s_1 s_0$

 

An analogous case exists for a static 0 hazard in a product of sums expression

Dynamic hazards are much more difficult to analyze, and occur in multi-level logic and where multiple inputs may change concurrently.

Handwritten notes in green ink include a large bracket on the right side, the text ".8 ns" in the middle, and a circled "C/L" at the bottom right.