


ECE 3060
VLSI and Advanced Digital Design

Hazards

Motivation


Suppose we wish a logic signal (say a DRAM $\overline{\text{WE}}$ signal) to be glitch free

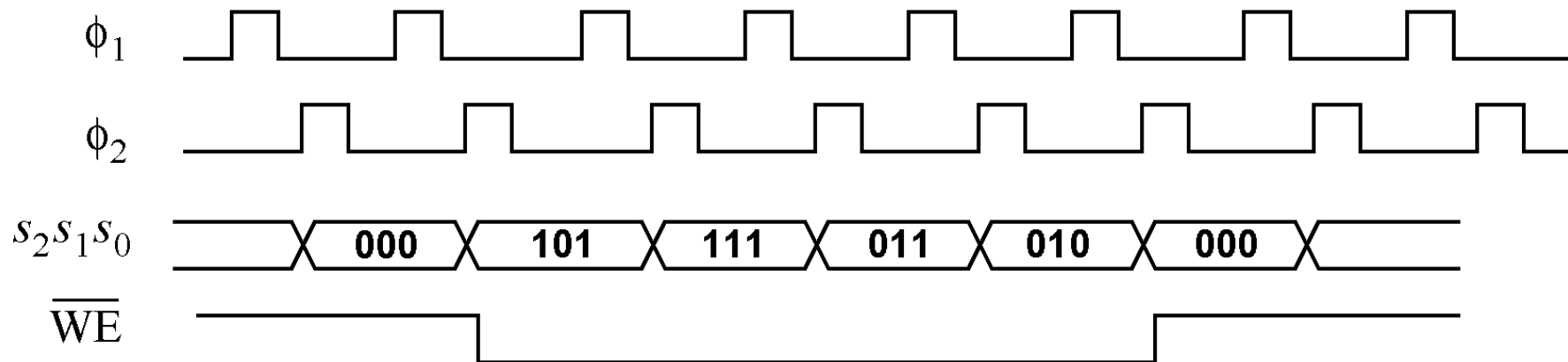Suppose the signal is generated by four states of a state machine as shown



Minimization yields $\overline{\text{WE}} = \overline{(s_2s_0 + \overline{s_2}s_1)}$


Implementation

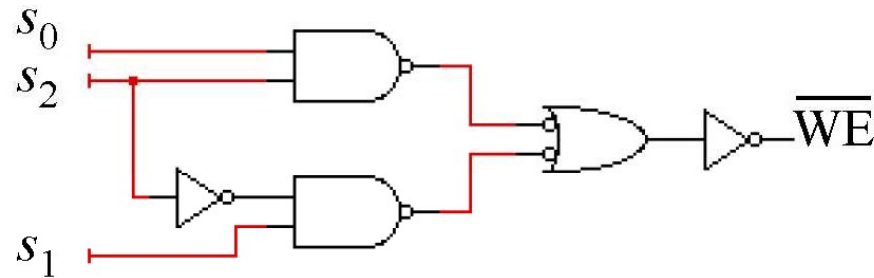

Consider transition $S = 111$ to $S = 011$


This cause of this glitch is a static 1 hazard in the implementation.

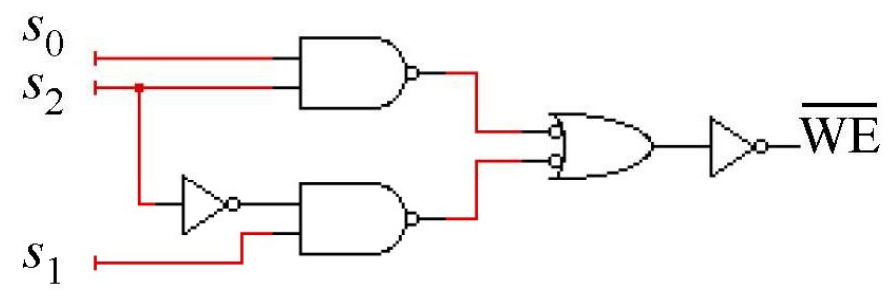A static 1 hazard is present whenever adjacent 1 nodes on the cube are not covered by the same implicant



Solution

Add the consensus term $s_1 s_0$

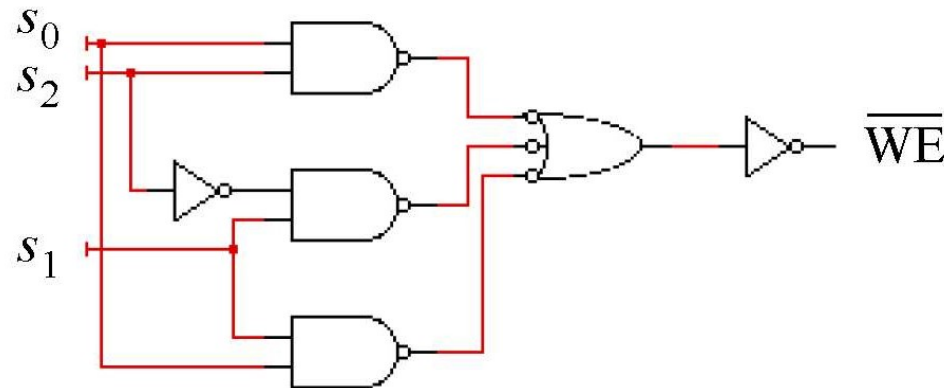

An analogous case exists for a static 0 hazard in a product of sums expression

Dynamic hazards are much more difficult to analyze, and occur in multi-level logic and where multiple inputs may change concurrently.