

Masking Countermeasures in Cryptographic Hardware: Part II

Cryptographic Hardware for Embedded Systems

ECE 3170

Fall 2025

Assoc. Prof. Vincent John Mooney III

Georgia Institute of Technology

Reading

- This lecture is based on three sources:
- Chapter 9 of *Power Analysis Attacks: Revealing the Secrets of Smart Cards* by Mangard et al., 2007, ISBN-13: 978-0-387-30857-9, ISBN-10: 0-387-30857-1, e-ISBN-10: 0-387-38162-7.
- T. Popp and S. Mangard, “Masked Dual-Rail Pre-charge Logic: Differential Power Analysis Resistance Without Routing Constraints,” Cryptographic Hardware for Embedded Systems (CHES) conference, 2005.
- Chapter 2 of *Handbook of Applied Cryptography* by Menezes et al., 1996, ISBN: 978-1-119-09672-6.

Motivation

- Prior approaches (such as WDDL) attempt to consume a constant amount of energy regardless of logic transition
 - Basis: same number of wires transition from one logic value (0 or 1) to the opposite
- A major problem with prior work is that semi-custom chip design tools place and route standard cell logic gates without guaranteeing that all wires have equivalent capacitive loads
 - Furthermore, there does not appear to be any straightforward manner to do so

Recall Slide 30 of Lecture 26 Hiding II

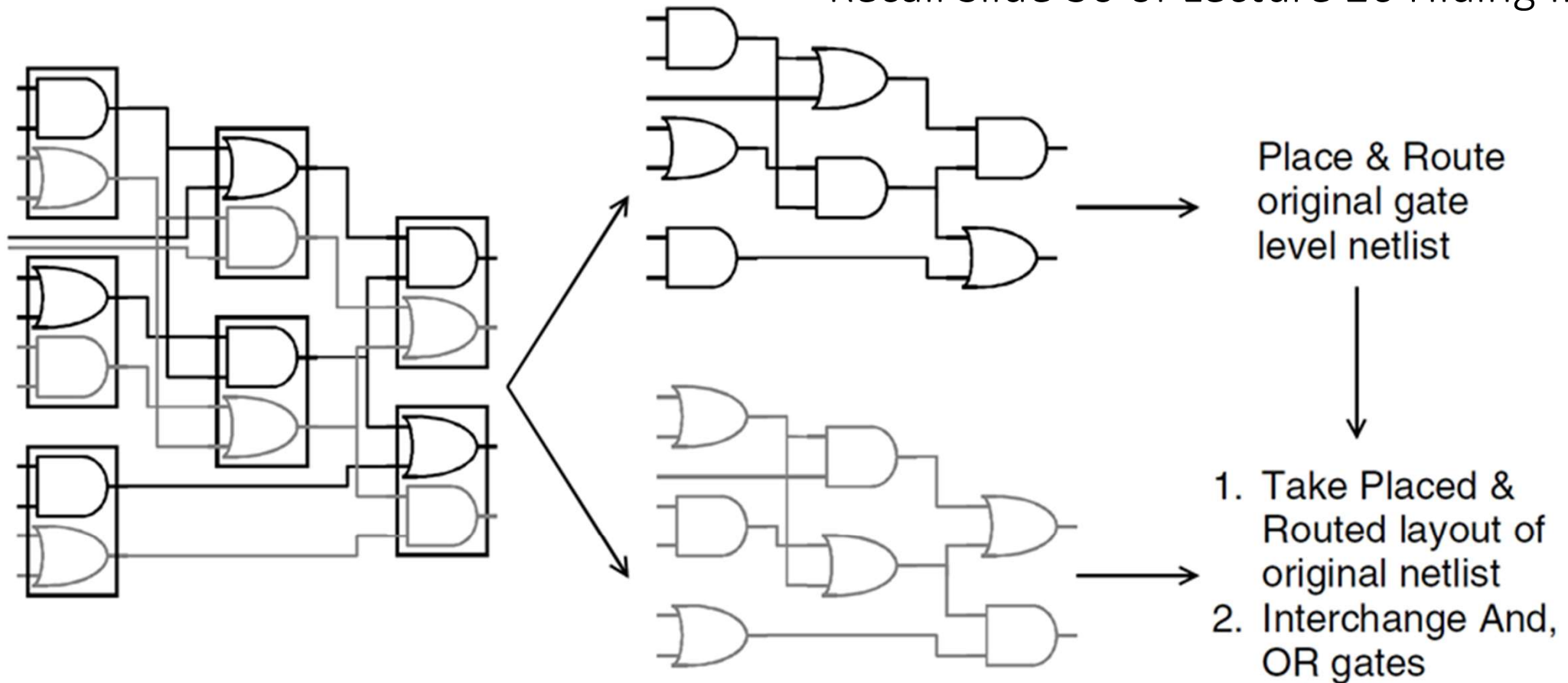


Fig. 5. Derivation of Divided WDDL

Masked Dual-rail Precharge Logic (MDPL)

Table 1. Transitions of the value d of a node in a CMOS

d_{t-1}	d_t	Energy Probability	
0	0	E_{00}	p_{00}
0	1	E_{01}	p_{01}
1	0	E_{10}	p_{10}
1	1	E_{11}	p_{11}

Expected Value of the Difference of the Means

$$\mathcal{E}(DM_{d_t}) = \mathcal{E}(M_{d_t=1}) - \mathcal{E}(M_{d_t=0}) = \frac{p_{11}E_{11} + p_{01}E_{01}}{p_{11} + p_{01}} - \frac{p_{00}E_{00} + p_{10}E_{10}}{p_{00} + p_{10}}$$

Idea

- In standard CMOS logic, $E_{00} \approx E_{11} \ll E_{10} \neq E_{01}$
- Prior approaches fail to guarantee $E_{00} = E_{11} = E_{10} = E_{01}$
- Therefore, another approach is to mask the value of d
 - Instead of representing d by two wires for each polarity $\bar{d}$ and d
 - Generate a random mask m and update m every clock cycle
 - $d_m = d \oplus m$

Table 2. Transitions of the value d_m of a masked node

Line no.	d_{t-1}	m_{t-1}	$d_{m_{t-1}}$	d_t	m_t	d_{m_t}	Energy	Probability
1	0	0	0	0	0	0	E_{00}	$\frac{1}{4}p_{00}$
2	0	0	0	1	1	0	E_{00}	$\frac{1}{4}p_{01}$
3	1	1	0	0	0	0	E_{00}	$\frac{1}{4}p_{10}$
4	1	1	0	1	1	0	E_{00}	$\frac{1}{4}p_{11}$
5	0	0	0	0	1	1	E_{01}	$\frac{1}{4}p_{00}$
6	0	0	0	1	0	1	E_{01}	$\frac{1}{4}p_{01}$
7	1	1	0	0	1	1	E_{01}	$\frac{1}{4}p_{10}$
8	1	1	0	1	0	1	E_{01}	$\frac{1}{4}p_{11}$
9	0	1	1	0	0	0	E_{10}	$\frac{1}{4}p_{00}$
10	0	1	1	1	1	0	E_{10}	$\frac{1}{4}p_{01}$
11	1	0	1	0	0	0	E_{10}	$\frac{1}{4}p_{10}$
12	1	0	1	1	1	0	E_{10}	$\frac{1}{4}p_{11}$
13	0	1	1	0	1	1	E_{11}	$\frac{1}{4}p_{00}$
14	0	1	1	1	0	1	E_{11}	$\frac{1}{4}p_{01}$
15	1	0	1	0	1	1	E_{11}	$\frac{1}{4}p_{10}$
16	1	0	1	1	0	1	E_{11}	$\frac{1}{4}p_{11}$

$$\mathcal{E}(M_{d_t=0}) = \mathcal{E}(M_{d_t=1}) = \frac{1}{4} (E_{00} + E_{01} + E_{10} + E_{11})$$

Masked Dual-rail Pre-charge Logic: MDPL

- Every signal masked with same random value m
- AND gate in MDPL
- Consider inputs a_m and b_m
 - Recall $a_m = a \oplus m$ and $b_m = b \oplus m$
 - Also $a = a_m \oplus m$ and $b = b_m \oplus m$
- $q = ab \Rightarrow q_m = q \oplus m = ab \oplus m$
- $\Rightarrow q_m = (a)(b) \oplus m$
- $\Rightarrow q_m = (a_m \oplus m)(b_m \oplus m) \oplus m$
- Similarly, $\overline{q}_m = (\overline{a}_m \oplus \overline{m})(\overline{b}_m \oplus \overline{m}) \oplus \overline{m}$

Table 3. Truth table of an MDPL AND gate

Line no.	a_m	b_m	m	q_m	$\overline{a}_m$	$\overline{b}_m$	$\overline{m}$	$\overline{q}_m$
1	0	0	0	0	1	1	1	1
2	0	0	1	0	1	1	0	1
3	0	1	0	0	1	0	1	1
4	0	1	1	1	1	0	0	0
5	1	0	0	0	0	1	1	1
6	1	0	1	1	0	1	0	0
7	1	1	0	1	0	0	1	0
8	1	1	1	1	0	0	0	0

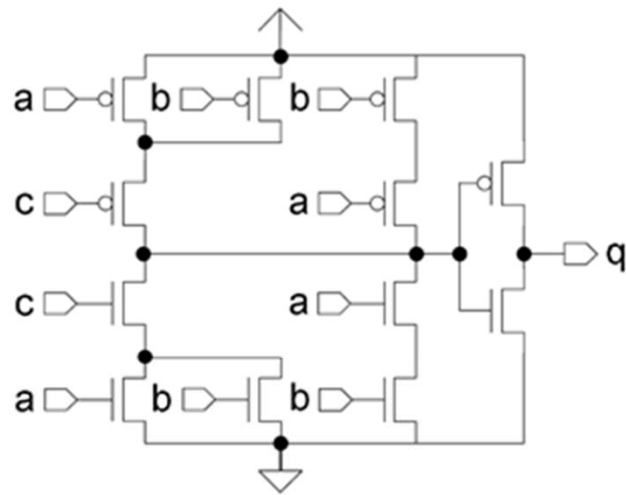


Fig. 1. Schematic of a CMOS majority gate

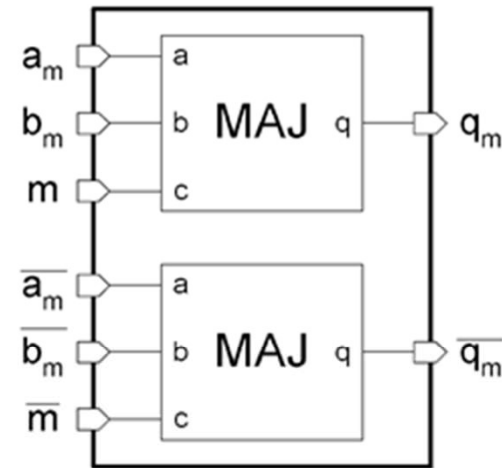


Fig. 2. Schematic of an MDPL AND gate

MDPL Operation

- As with WDDL, inversion is implemented by switching wires
- An MDPL gate for OR can also be used (not shown, see reference)
- Precharge wave sets all values to zero
 - Note that for a_m , $\overline{a_m}$, b_m , $\overline{b_m}$, m and $\overline{m}$ all equal to zero makes q_m and $\overline{q_m}$ zero
- During the evaluation phase, the majority gates each make at most one transition (from 0 to 1 since they are all precharged to zero!)
- Majority gates are available in all standard cell libraries known

Table 5. MDPL cells and their CMOS implementations

MDPL cell	CMOS implementation of MDPL cell	Area (gate equivalents) of		Ratio $\frac{MDPL}{CMOS}$
		MDPL cell	std. CMOS cell	
Inverter	Wire swapping	0	0.67	0
Buffer	2×Buffer	2	1	2
AND, OR (2-in)	2×MAJ (3-in)	4	1.67	2.4
NAND, NOR (2-in)	2×MAJ (3-in)	4	1	4
XOR (2-in)	6×MAJ (3-in)	12	2.33	5.1
XNOR (2-in)	6×MAJ (3-in)	12	2	6
D-Flip-Flop	2×AND, 2×OR (both 2-in)			
	2×MAJ (3-in), 1×D-FF	17.67	5	3.5

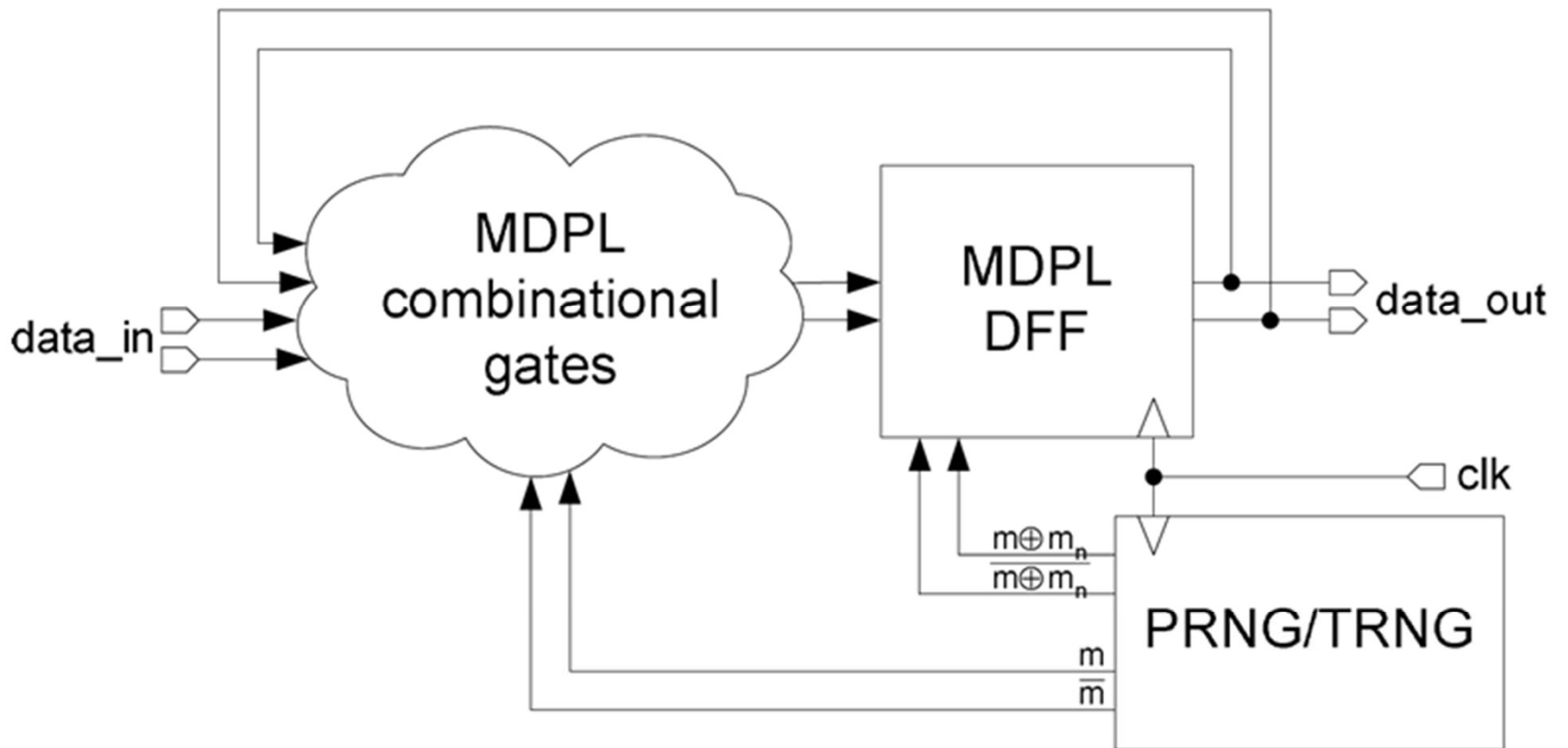


Fig. 5. Architecture of an MDPL circuit

RECALL:
Hiding II
Slide 30!

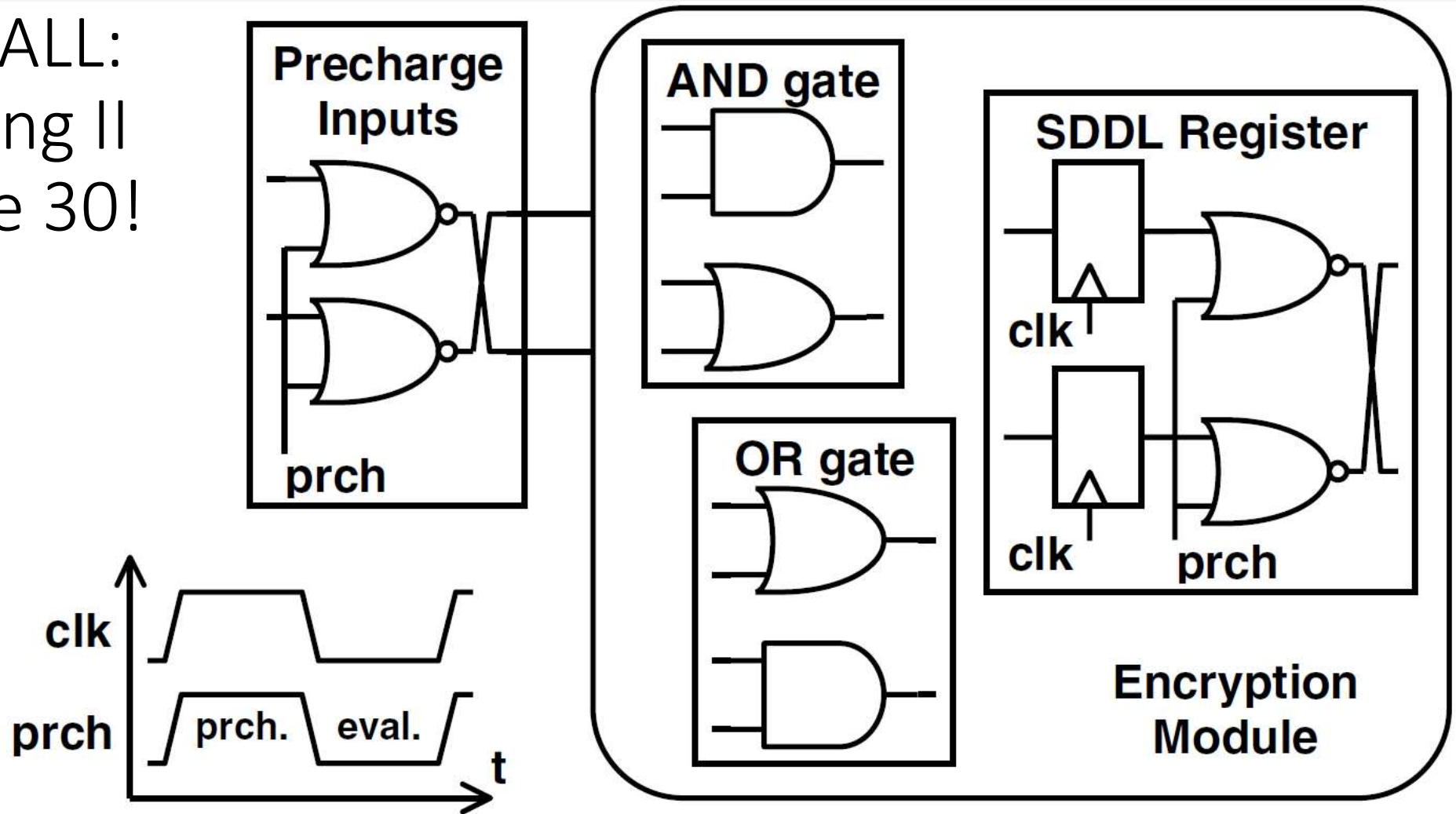


Fig. 3. Precharge wave generation with SDDL FF's

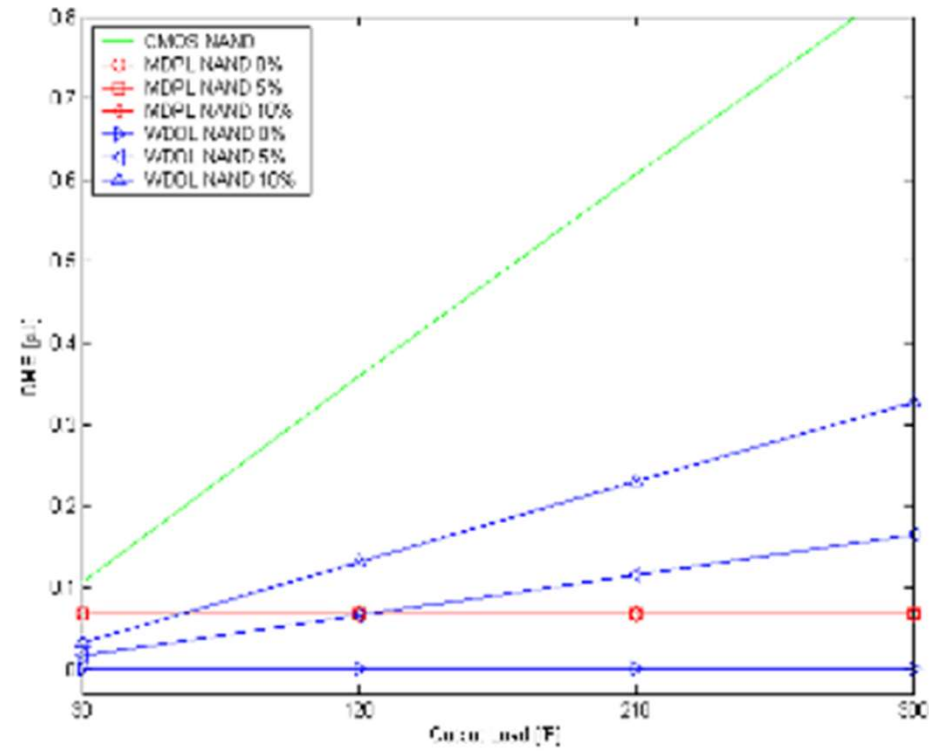


Fig. 6. Comparison of the DME of CMOS, WDDL and MDPL implementations NAND gate

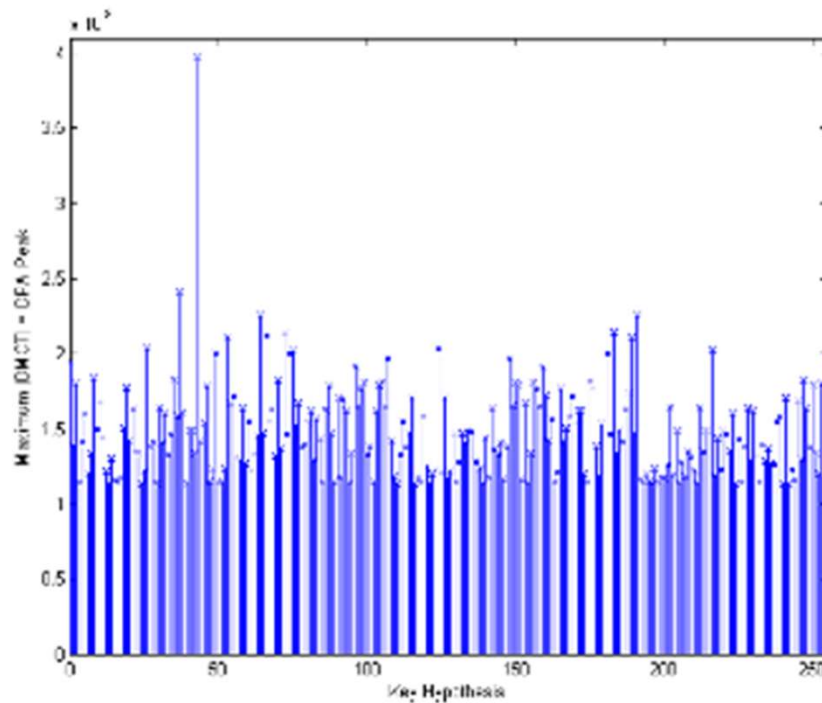


Fig. 7. DPA peaks for all key hypothesis for a DPA attack on an AES implemented in CMOS

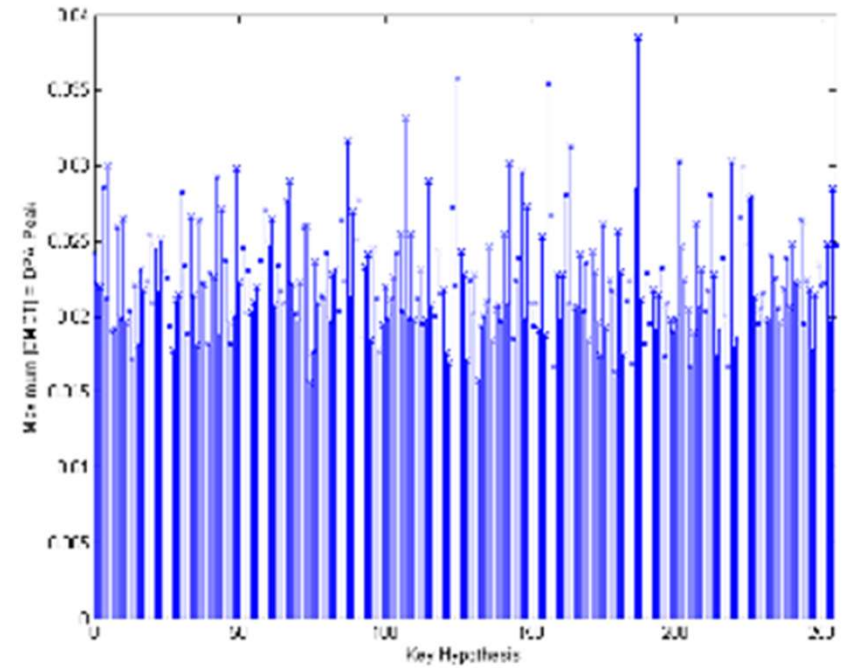


Fig. 8. DPA peaks for all key hypothesis for a DPA attack on an AES implemented in MDPL

Table 6. Comparison of AES implementations in CMOS and MDPL

	CMOS	MDPL	Ratio $\frac{MDPL}{CMOS}$
Area (gate equivalents)	3628	16465	4.54
Speed (MHz; worst-case speed corner)	16.91	9.82	0.58

Conclusion